

# Digital Design, Group Project

## EENG 28010

Course Overview - Introduce Assignment 2

Dr Faezeh Arab Hassani and Dr Shuangyi Yan

Dept of Electrical and Electronic Engineering



# Unit Goals

- ❑ To gain experience in digital design using VHDL and FPGA prototyping
- ❑ To familiarize with related industry standard tools
- ❑ To work in a team to design a digital system and implement it in an FPGA




# Outline

- ❑ Introduction of Assignment 2
- ❑ Writing Synthesisable Code

 
# Assignment 2: Peak Detector

**Specification:** To design, build and test a peak detector which is under the control of a computer. The system captures up to 500 8-bit digital samples from a source.



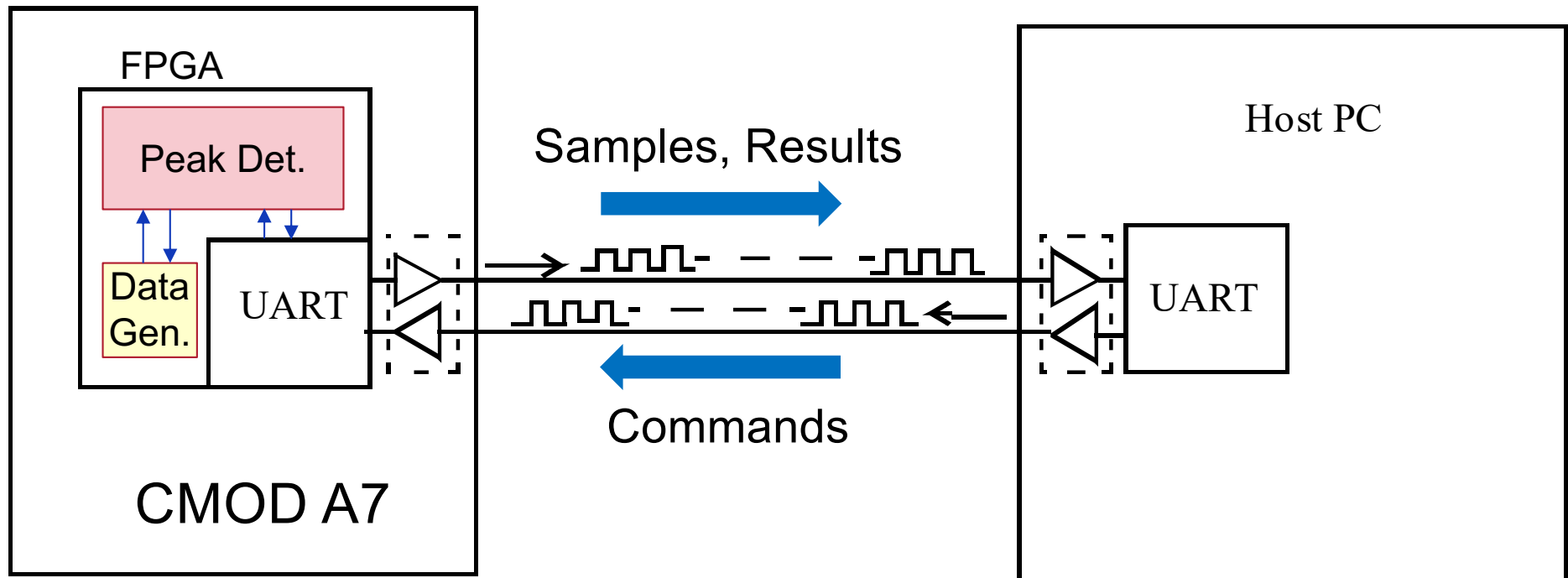
# Peak Detector – Serial Communication with PC via UART

- ❑ User commands accepted from PC and outputs printed to the PC
- ❑ Serial communication implemented by Universal Asynchronous Receiver Transmitter (UART)


 
# Capturing samples


Capture seven points around the highest peak; 3 each side.



# Main Requirements

- ❑ Receive commands through UART from a computer terminal
  - UART demo is provided
  - Ascii code for printing text in the terminal
- ❑ Request amount of data based on commands
  - “aNNN” or “ANNN”
  - Display/print all data
- ❑ Analysis peak data and capture the adjacent samples
- ❑ Send the data and results back to the computer terminal through UART
  - “P” or ”p”
  - “L” or ”l”


# Function requirements

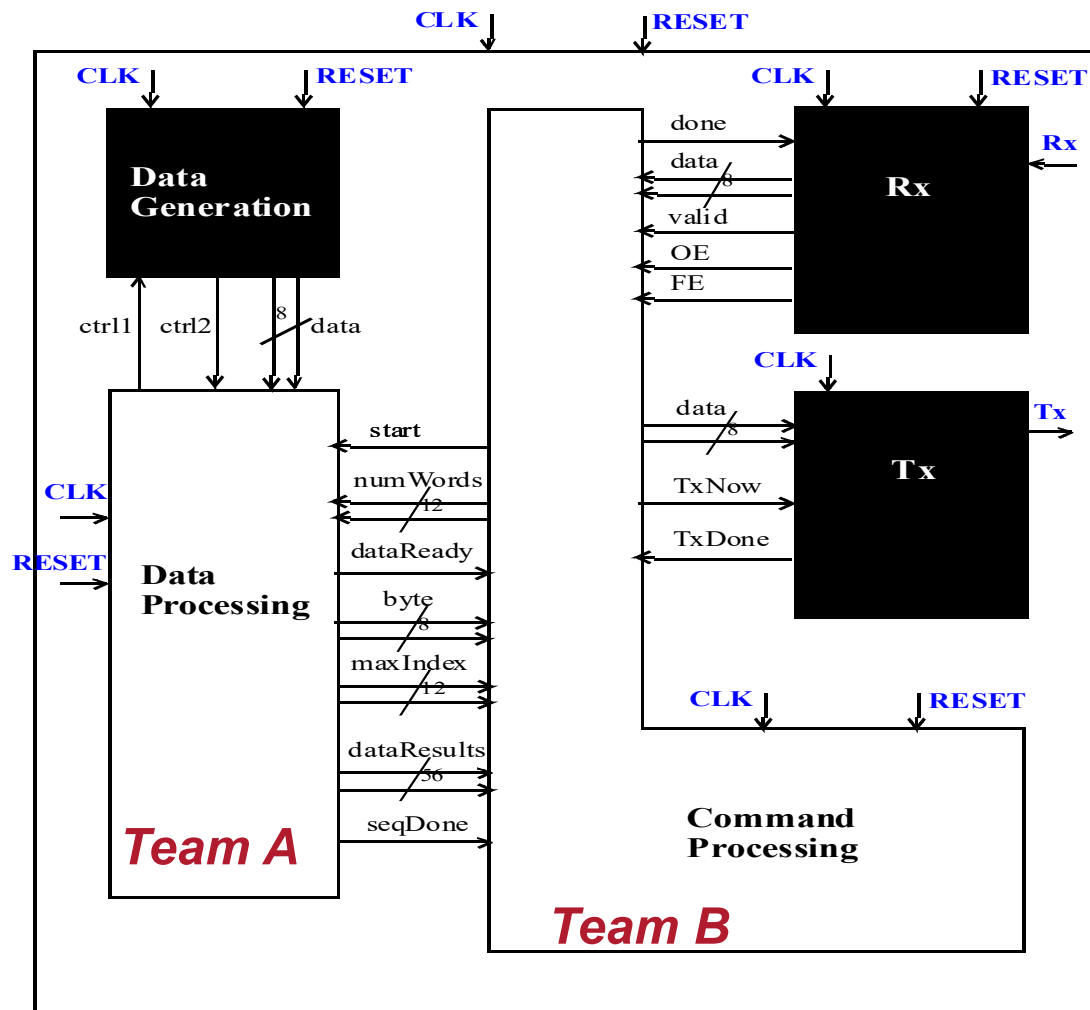

- ❑ Data Generator, Tx and Rx has been provided
- ❑ Encrypted solutions for individual testing
  - Data Processor
  - Command Processor
- ❑ Data Processor
- ❑ Command Processor
- ❑ Integration simulation
- ❑ Synthesis and Implementation




# Data Processor

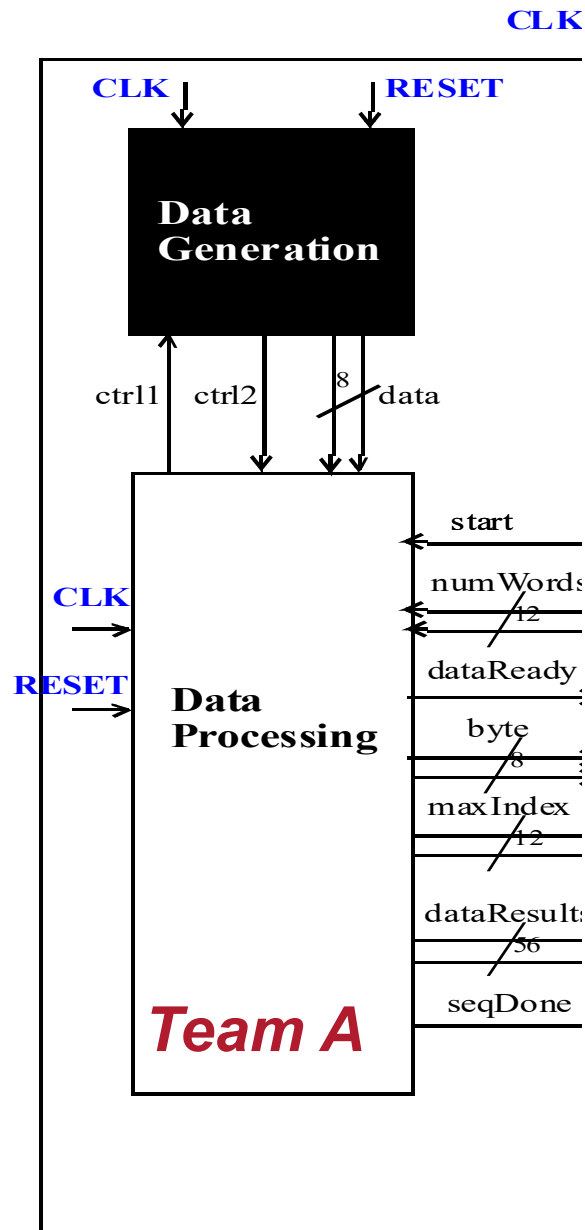

- ❑ "start": sync data processor and command processor
- ❑ Read requirements from CMD processor
- ❑ "ctrl 1" and "ctrl 2": request data
- ❑ "dataReady": inform CMD processor to read data
- ❑ Analysis peak and store samples:
  - Peak and other 6 samples
  - Provide results


# Command Processor

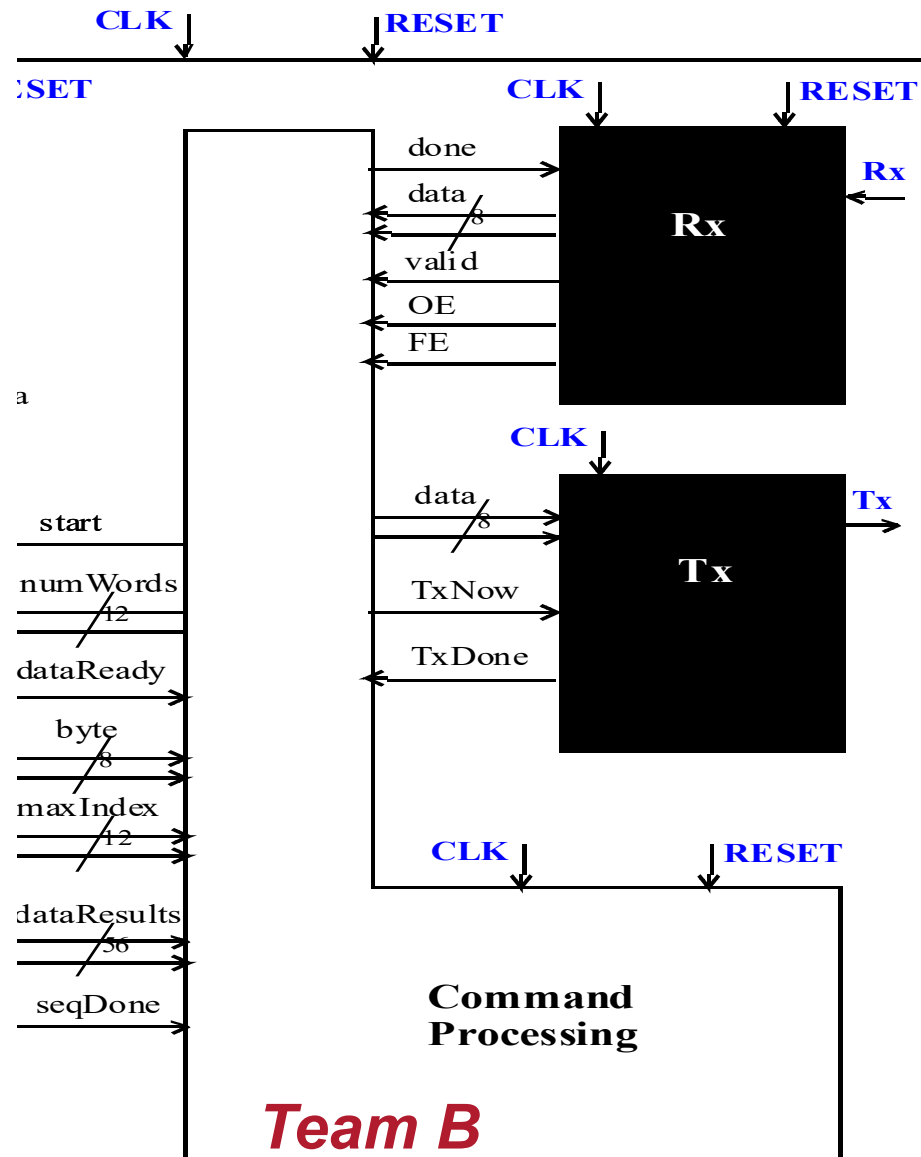

- ☐ Manage UART links
- ☐ CMD validation
- ☐ Request data from Data Processor
- ☐ Print all input commands, results for different commands
  - Send the ASCII code to Tx
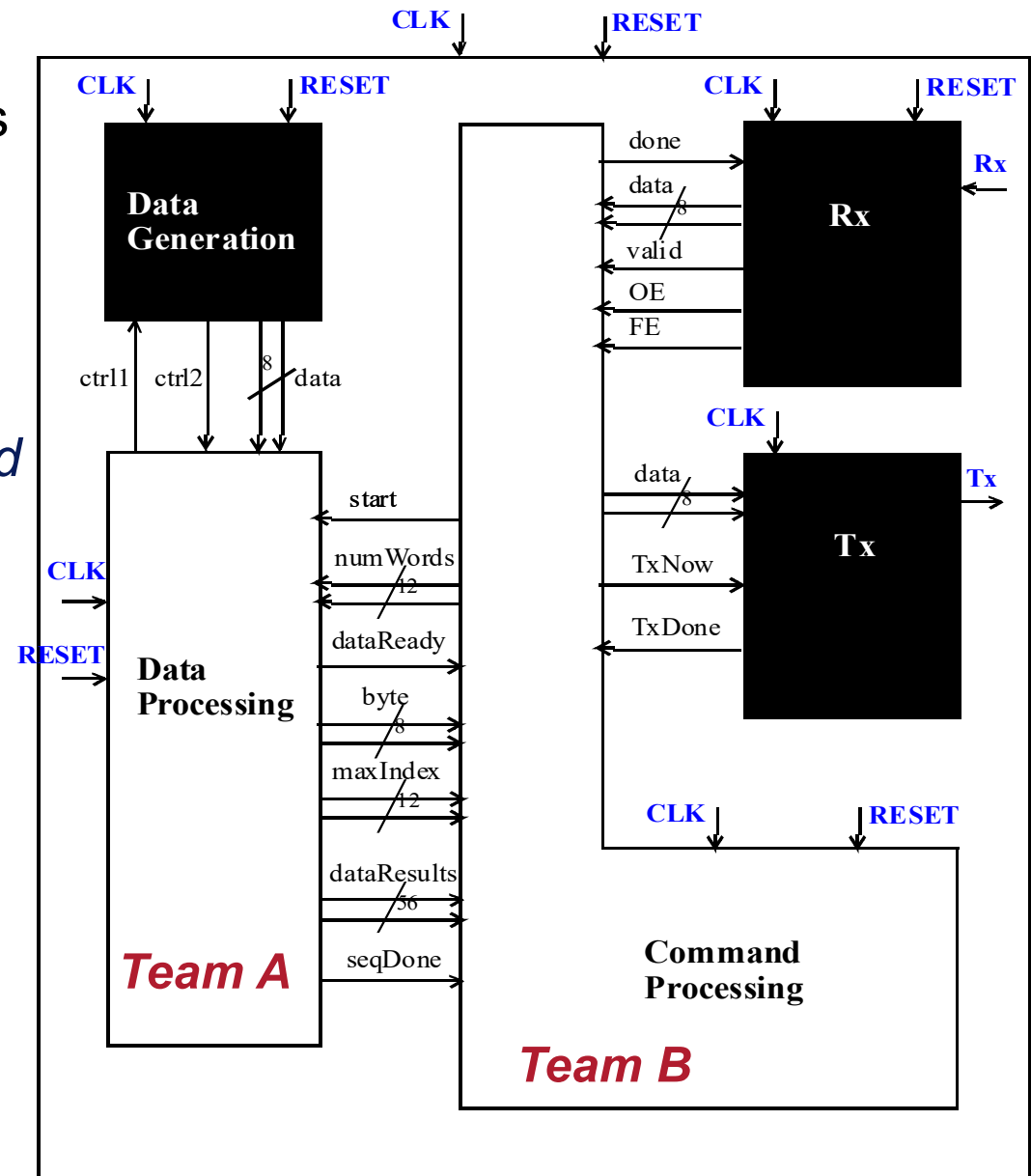
# Peak Detector – Work Plan

- ❑ Divide group into two sub teams
- ❑ **Team A** works on the *Data Processing* block (two members)
- ❑ **Team B** works on the *Command Processing* block (three members)
- ❑ Clearly defined interface and black box implementations of Data Processor / Command Processor allow independent development



# Signed vs. Unsigned implementation

**Odd team number: unsigned implementation**

**Even team number: signed implementation**

- ❑ If your group number is odd, you should treat the bytes delivered by the data source as unsigned.
- ❑ If your group number is even, you should treat the bytes delivered by the data source as signed.
  
- ❑ Affect data processor design
  - comparison between two values

# Live Demo

# Use knowledge learnt in Assignment 1

- ❑ Building FSM diagram
- ❑ Using D Flip-Flops
- ❑ Synchronous system
  - using x-reg to hold its value
  - detecting edges and applying it in assignment 2
  - Synchronizing two modules with “start” and “dataReady”
- ❑ Understanding how to design a system comprising a datapath and controller

# Suggested Approach

- ❑ Try both demo and simulation
- ❑ Start from the FSM diagram
- ❑ Separation of the combinatorial logic with state machine
- ❑ List all the functions need to by synchronized to the clock
- ❑ Manage handshaking protocol between all units
- ❑ Use the testbench efficiently
  - You can customize it for your testing.
- ❑ Get rid of all the latches we are encountered while synthesizing the code.

Odd group number: unsigned implementation

Even group number: signed implementation

# Week 16 - 17

## ❑ Start with UART demo

- Understand the counters used in both Tx and Rx
- Watch video explanation about TX/RX implementation

## ❑ Understand the whole system

- Read lab note for the system requirements
- Analysis simulation results based on the provided codes
- Watch the two-phase signaling protocol


## ❑ Work on FSM charts

- Feedback on charts will be provided on week 19 (Group A) and week 21 (Group B) per group
- Team meeting with all team members (required full attendance)



# Peak Detector – Work Plan (*cont.*)

- ❑ Task 1: Command Processing and Data Processing modules should work independently and satisfy specifications according to a software testbench
- ❑ Task 2: Integrate Cmd Proc and Data Proc to realise the full working design and validate by full system simulation and FPGA implementation

 

**Week 16 – 21 (4 Weeks):** Complete design of data processor and command processor. Prepare drafts for your individual chapter.

**Week 22:** Integration and testing individual components

**Week 23:** System integration, simulation and report

# Deadline and Marking

<i>Assignment 2: Design of a Peak Detector</i>	Final Design	Group Assignment	Submit code and group report	13:00 Thursday 28 April	65%
--	-----------------	---------------------	---------------------------------	-------------------------------	-----

Assignment 2: (In total: 65%) Including below sections:

- ☐ Report: 20% for all members
- ☐ Peer assessment: 5%
- ☐ Code:
  - Individual marking of Data processing and Command processing (30%), Team A and B get individual marks
  - Data processing and Command processing integration marking (10%) for all members

# Submission Package

- ❑ VHDL code for the whole system (40%)
  - Data Processor
  - Command Processor
  - Any developed modules
- ❑ Team report (20%)
- ❑ Peer assessment (5%), to be included in your team report

# Report Contents

- ❑ Around 10-15 pages
- ❑ Chapter 1: Description of the group composition and task division between group members.
  - Each student needs to summarize their contributions.
- ❑ Chapter 2: Design and simulation of Data Processing module including a block-level sketch of the main logic components and a state diagram (FSM or ASM) (Sub Team A)
- ❑ Chapter 3: Design and Simulation of Command Processing module including a block-level sketch of the main logic components and a state diagram (FSM or ASM) (Sub Team B)
- ❑ Chapter 4: Description of the system integration and test of your final implementation on FPGA.
  - Readable screenshots with description should be provided to demonstrate the required functions.
- ❑ Peer Assessments

# FPGA Collection and Return

- ❑ One FPGA per group
  - collect today or after class at MVB 4.23
  
- ❑ Return deadline: May 5th, 2023 to
  - MVB 4.23

# Group Work

## □ Sharing Work

- Two teams in each group for cmd and data procs
- Within each team, have tasks defined along structural lines
- Don't..
  - Allocate one person for simulation and one for synthesis
  - Allocate one person for debugging only or writing TBs
  - Have one person loosely associated with both teams for e.g., trouble-shooting
  - Above are all excuses for not doing fair share
  - Change roles and responsibilities of a group member without consultation within group

# Group Work

## □ Planning

- Do...
  - Have a project plan with timelines, milestones and regular meetings
  - Have a record of who does what and minutes of group meetings
  - These feed into interim report
  - Use official e-mail and agree on platform for information exchange

## □ Difficulties with group members


- Try to resolve through a conversation
- If it doesn't work, talk to Shuangyi or Faezeh.
- Don't...
  - Ignore issues until last moment

# Outline


- ❑ Assignment 2
- ❑ Writing Synthesisable Code
  - Generating hardware from code constructs
  - Type conversion
  - Avoiding unwanted latches



# FPGA Structure

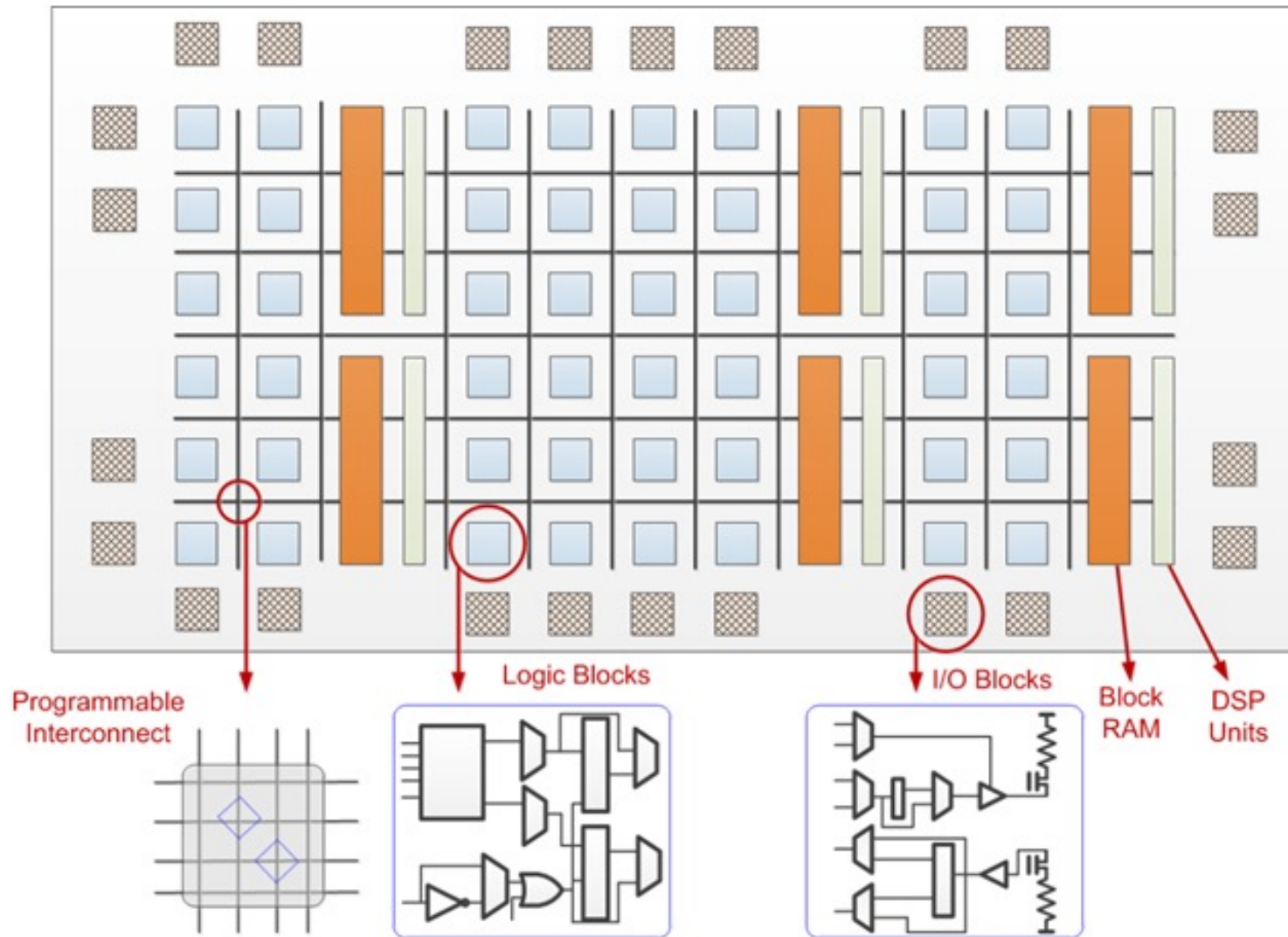


# Configurable logic block

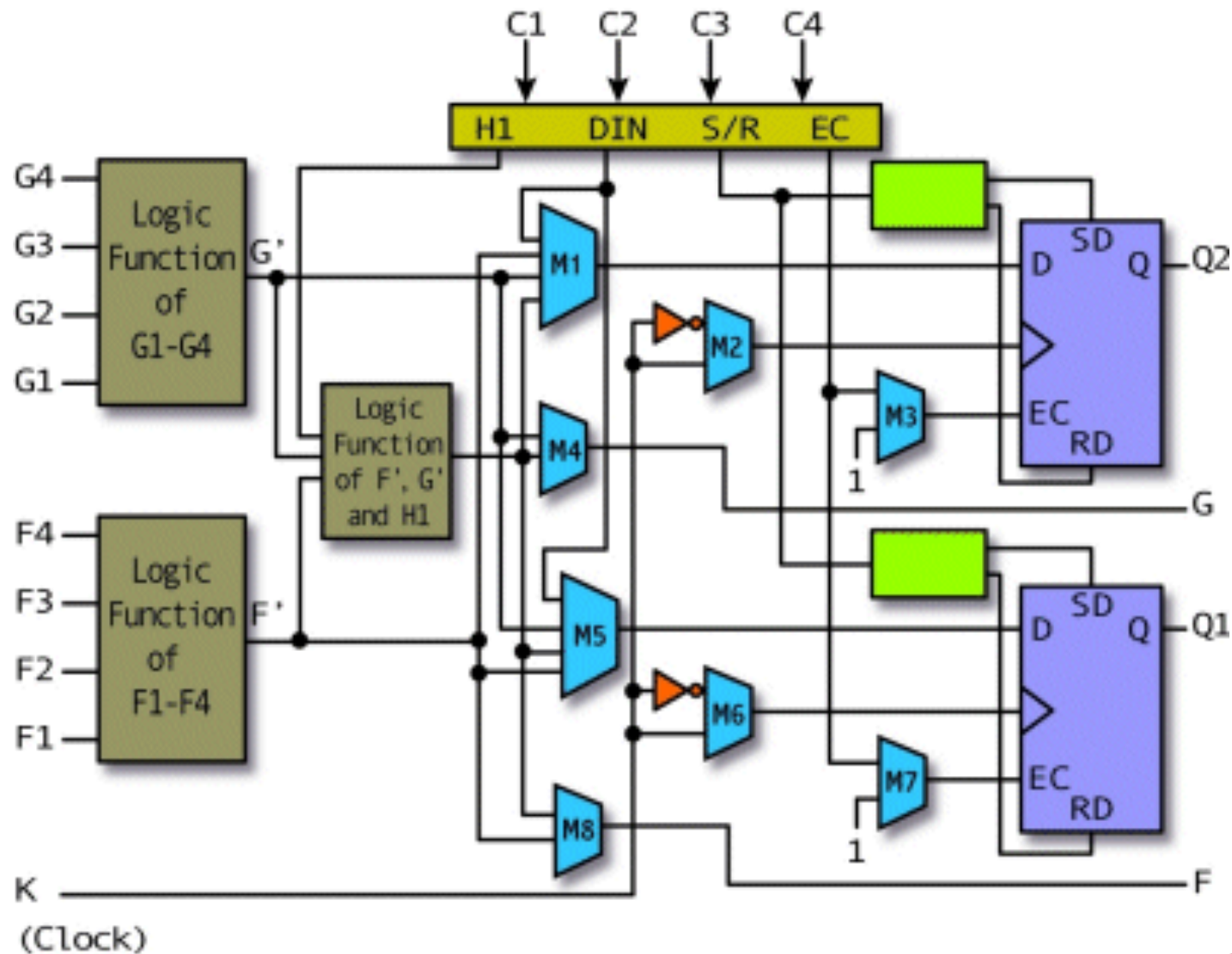

 
# Basic architecture of sequential logics

Three blocks:


- ❑ **State register:** a collection of D FFs controlled by the same clock signal
- ❑ **Next-state logic:** Combinational logic determine new value of the registers
- ❑ **Output logic:** combinational logic to generate output signals



# Mealy and Moore Machines

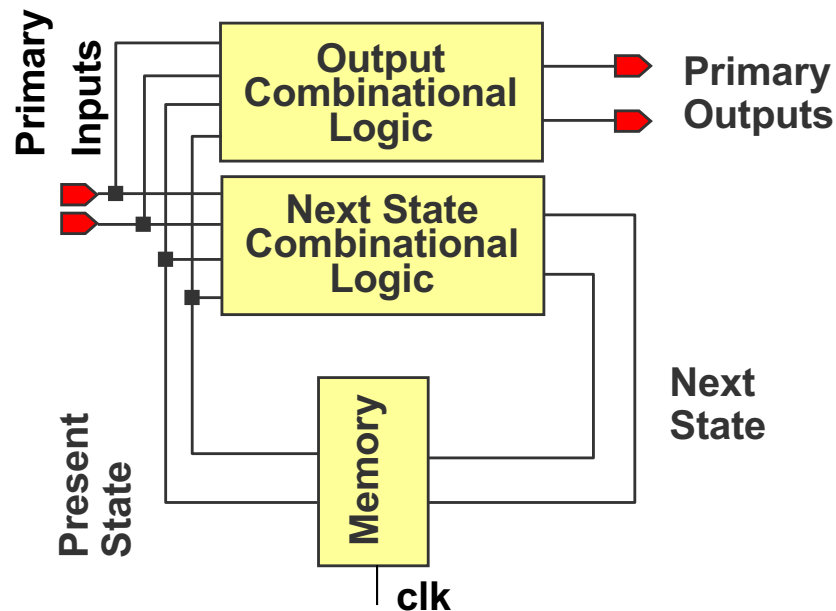

Mealy Machine

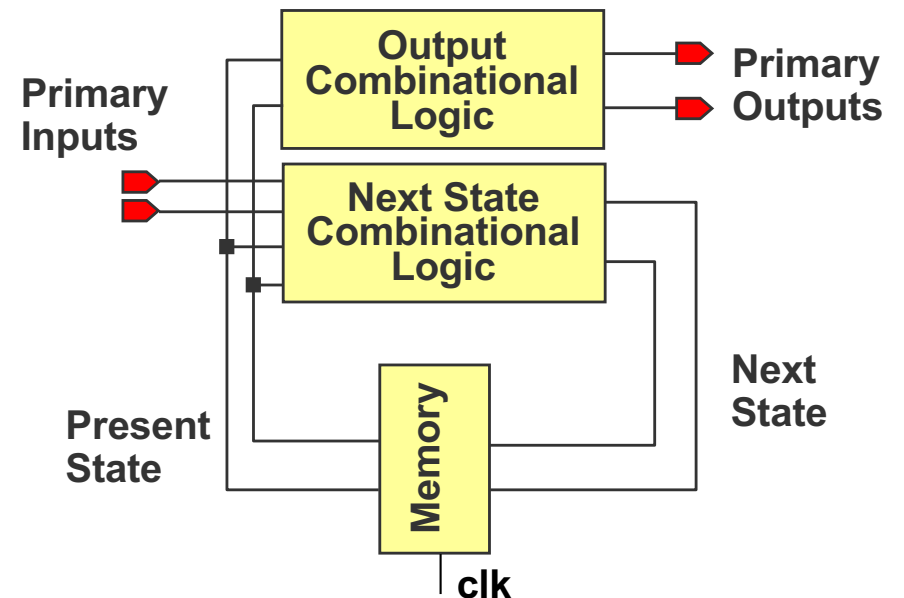

Moore Machine

- ❑ Most straightforward way to synthesise a state machine is to use a process for each function
  - next state (combinational)
  - output (combinational)
  - memory (sequential)

# Modelling a Mealy Machine

```
entity pattern_recog is
port ( X      : in  bit;
      CLK     : in  bit;
      RESET   : in  bit;
      Y       : out bit );
end;
```

```
seq: process (clk, reset)
begin
  if reset = '0' then
    CURRENT_STATE <= S0;
  elsif clk'event AND clk='1' then
    CURRENT_STATE <= NEXT_STATE;
  end if;
end process; -- seq
```

**State register**

```
combi_output: process(CURRENT_STATE, X)
begin
  case CURRENT_STATE is
    when S0 =>
      Y <= 0;    ....
               ....
               ....
```

**Output logic**

## Next-state logic

```
combi_nextState: process(CURRENT_STATE, X)
begin
  case CURRENT_STATE is
    when S0 =>
      if X='0' then
        NEXT_STATE <= S1;
      else
        NEXT_STATE <= S0;
      end if;

    when S1 =>
      if X='0' then
        NEXT_STATE <= ?;
      else
        ....

    when Sn =>
      if X='0' then
        NEXT_STATE <= ?;
      else
        NEXT_STATE <= ?;
      end if;

  end case;
end process; -- combi_nextState
```

# Unsigned and Signed Types

*Source: ref [4]*

- ❑ Used to represent numeric values:

<u>TYPE</u>	<u>Value</u>	<u>Interpretation</u>
unsigned	0 to $2^N - 1$	
signed	$-2^{(N-1)}$ to $2^{(N-1)} - 1$	2's Complement

- ❑ Usage similar to std\_logic\_vector:

```
signal A      : unsigned (3 down to 0);
signal B      : signed (3 downto 0);
signal C      : std_logic_vector (3 downto 0);
....
A <= "1111";   -- decimal 15
B <= "1111";   -- decimal -1
C <= "1111";   -- decimal 15 if using std_logic_unsigned
                -- (Synopsys library which extends std_logic_arith)
```

# Synthesis Support for Numeric Operations

*Source: ref [4]*

- ❑ Generally, if the `numeric_bit` and `numeric_std` packages are supported, the operators within them are supported
- ❑ Arithmetic operators - “`abs`”, “`+`”, “`-`”, “`*`”, “`/`”, “`rem`”, “`mod`”
- ❑ Comparison operators - “`>`”, “`<`”, “`<=`”, “`>=`”, “`=`”, “`/=`”
- ❑ Shift functions: “`shift_left`”, “`shift_right`”, “`rotate_left`”, “`rotate_right`”, “`resize`”
  - Use these library defined functions rather than the built-in VHDL constructs “`sla`”, “`sra`”, “`sll`” etc for shifting and concatenation
- ❑ Conversion functions: “`to_integer`”, “`to_unsigned`”, “`to_signed`”
- ❑ `use ieee.numeric_std.all;`

# Packages for Numeric Operations

*Source: ref [4]*

- ❑ All synthesis tools support some type of arithmetic packages
- ❑ Synopsys developed packages based on std\_logic\_1164 package - supported by many other synthesis tools
  - std\_logic\_arith
  - std\_logic\_signed
  - std\_logic\_unsigned
- ❑ Actel synthesis tools support their own package
  - asy1.arith
- ❑ IEEE has developed standard packages for synthesis IEEE Std. 1076.3
  - Numeric\_Bit
  - Numeric\_Std

use IEEE.STD\_LOGIC\_ARITH.all

use one or  
the other,  
never both

use IEEE.NUMERIC\_STD.all

Recommendation:  
For new design, use numeric\_std



# Overloading Examples

*Source: ref [4]*

```
signal A_uv, B_uv, C_uv, D_uv, E_uv : unsigned(7 downto 0) ;
signal R_sv, S_sv, T_sv, U_sv, V_sv : signed(7 downto 0) ;
signal J_slv, K_slv, L_slv : std_logic_vector(7 downto 0) ;
signal Y_sv : signed(8 downto 0) ;
...
-- Permitted
A_uv <= B_uv + C_uv ; -- Unsigned + Unsigned = Unsigned
D_uv <= B_uv + 1 ;    -- Unsigned + Integer = Unsigned
E_uv <= 1 + C_uv;     -- Integer + Unsigned = Unsigned
R_sv <= S_sv + T_sv ; -- Signed + Signed = Signed
U_sv <= S_sv + 1 ;    -- Signed + Integer = Signed
V_sv <= 1 + T_sv;     -- Integer + Signed = Signed
-- only legal if using std_logic_unsigned (which you should not!)
J_slv <= K_slv + L_slv ;

-- Illegal Cannot mix different array sizes
Y_sv <= A_uv - B_uv; -- want signed result
-- Solution is to carry out type conversions
```

## Automatic Type Conversion: Unsigned, Signed $\Leftrightarrow$ std\_logic

*Source: ref [4]*

- ❑ Two types convert automatically when both are subtypes of the same type

```
SUBTYPE std_logic IS resolved std_ulogic;
```

- Converting between `std_ulogic` and `std_logic` is automatic

```
-- all legal
```

```
B_sul <= K_sv(7) ;
```

```
L_uv(0) <= C_sl ;
```

```
M_slv(2) <= N_sv(2);
```

```
Y_sl <= A_sl and B_sul and J_uv(2) and K_sv(7) and M_slv(2);
```

## Type Casting: Unsigned, Signed $\Leftrightarrow$ Std\_Logic\_Vector

*Source: ref [4]*

□ Use type casting to convert equal sized arrays when:

- Elements have a common base type (i.e., std\_logic)
- Indices have a common base type (i.e., Integer)

```
A_slv <= std_logic_vector( B_uv );  
C_slv <= std_logic_vector( D_sv );  
G_uv <= unsigned( H_slv );  
J_sv <= signed( K_slv );
```

-- Eg: unsigned – unsigned = signed

```
signal X_uv, Y_uv : unsigned (6 downto 0) ;  
signal Z_sv : signed (7 downto 0) ;
```

...

```
Z_sv <= signed('0' & X_uv) - signed('0' & Y_uv) ;
```

## Numeric\_Std Function Conversions: Unsigned, Signed <=> Integer

*Source: ref [4]*

- ❑ Converting to and from integer requires a conversion function

```
signal A_uv, C_uv : unsigned (7 downto 0) ;  
signal Unsigned_int : integer range 0 to 255 ;  
signal B_sv, D_sv : signed( 7 downto 0) ;  
signal Signed_int : integer range -128 to 127
```

-- unsigned, signed => integer

```
Unsigned_int <= TO_INTEGER ( A_uv ) ;  
Signed_int <= TO_INTEGER ( B_sv ) ;
```

Width of array

-- integer => unsigned, Signed

```
C_uv <= TO_UNSIGNED ( unsigned_int, 8 ) ;  
D_sv <= TO_SIGNED ( signed_int, 8 ) ;
```

-- Eg: indexing an array

```
Data_slv <= ROM( TO_INTEGER( Addr_uv) ) ;
```

# Avoid using latches

- ❑ Latches are generally "a bad thing" - unless you *really* know what you are doing.
- ❑ In synthesis, latches are not an error - they will be reported as either information or warning
- ❑ In mapping and place and route, you will not get any warnings - the mapping and place and route tools just do what the synthesis tool tells them to do!
- ❑ But you can often spot latches in the place and route summary, either as elements containing strings such as LD or DL; or explicitly listed as latches.

# Avoiding Latches

## □ Where do these evil latches come from?

- You directly instantiated them or inferred them in your code on purpose
  - Valid technique for meeting timing requirements in aggressive designs (e.g., borrowing time from the next cycle)
  - DO NOT PRACTICE IN THIS UNIT!
- You inferred them in your code by accident
  - In processes modelling combinational logic, all the signals on Right hand side (RHS) of assignment must appear in sensitivity list.
  - In processes modelling combinational logic, you have incompletely specified if-else or case statements, or read before assigning.
  - In processes modeling sequential logic, you have more than a single clock and asynchronous control in the sensitivity list.

# Inferring a Latch

```
ENTITY what IS
PORT (clk, d: IN std_logic;
      q: out std_logic);
END what;

ARCHITECTURE behav OF what IS
BEGIN
  PROCESS(clk, d)
  BEGIN
    IF clk = '1' THEN
      q <= d;
    END IF;
  END PROCESS;
END behav;
```

- ❑ VHDL semantics require that q retains its value over the entire simulation run
- ❑ Not assigned in each branch
- ❑ Latch inferred as assignment is under the control of a level-sensitive condition

**Do not use latches!**

# Mistakenly Inferring Latches with CASE


Latch Creation via Incomplete Assignment in Conditional Assignment:

- ❑ Not assigning all conditional expressions in a CASE structure

```
library IEEE;
use IEEE.std_logic_1164.all;

ENTITY mux3_seq is
  PORT(a      : IN  std_logic;
       b      : IN  std_logic;
       c      : IN  std_logic;
       sel    : IN  std_logic_vector(1 DOWNTO 0);
       y      : OUT std_logic);
END mux3_seq;
```
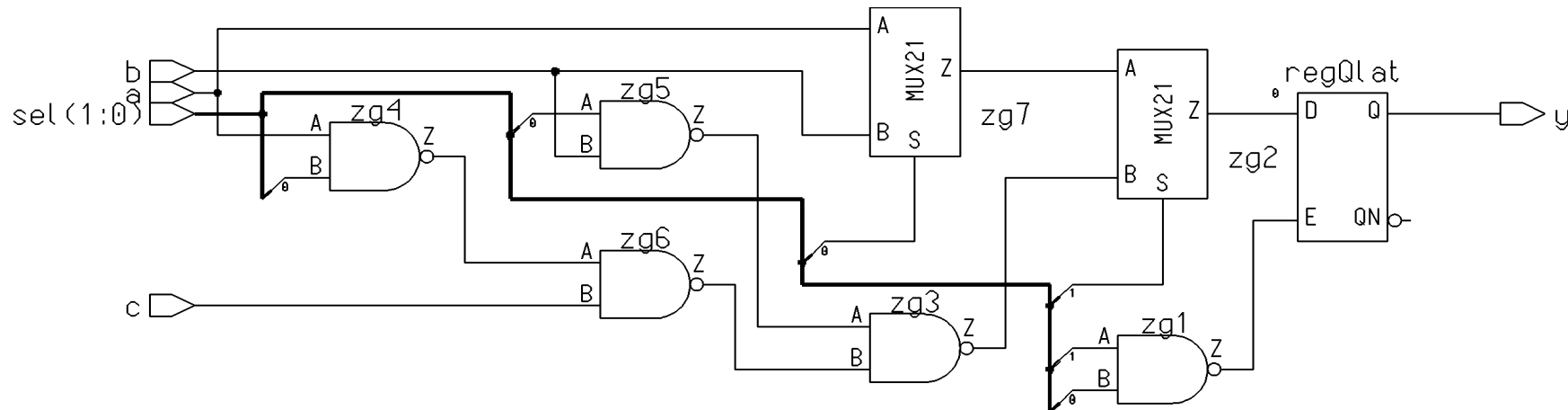
```
ARCHITECTURE behavior OF mux3_seq IS
  BEGIN
    comb : PROCESS(a,b,c,sel)
      BEGIN
        CASE sel IS
          WHEN "00" => y <= a;
          WHEN "01" => y <= b;
          WHEN "10" => y <= c;
          WHEN OTHERS => --empty
        END CASE;
      END PROCESS comb;
  END behavior;
```





# Avoiding Unwanted Latches


- ❑ Assigning values of “don’t care” (‘-’) in these cases can avoid unwanted latch inference

```
library IEEE;
use IEEE.std_logic_1164.all;

ENTITY mux3 is
  PORT (a      : IN  std_logic;
        b      : IN  std_logic;
        c      : IN  std_logic;
        sel    : IN  std_logic_vector(1 DOWNTO 0);
        y      : OUT std_logic);
END mux3;

ARCHITECTURE behavior OF mux3 IS

   BEGIN
    comb : PROCESS(a,b,c,sel)
    BEGIN
      CASE sel IS
        WHEN "00" => y <= a;
        WHEN "01" => y <= b;
        WHEN "10" => y <= c;
        WHEN OTHERS => y <= '-';
      END CASE;
    END PROCESS comb;
  END behavior;
```




**Latches are generated mostly by combinational logic!**

**Be careful when you are writing combinational code!**
 
# Wrong Implementation of a Counter

```
ENTITY incr IS
PORT (en: IN std_logic;
      z: out unsigned(0 to 1));
END incr;

ARCHITECTURE behav OF incr IS
BEGIN
  PROCESS(en)
    VARIABLE count: unsigned(0 to 1);
  BEGIN
    IF en = '1' THEN
      count := count + 1;
    END IF;
    z <= count;
  END PROCESS;
END behav;
```




**Do not use latches!**
 
# Correct Implementation of a Counter

```
ENTITY incr IS
PORT (en: IN std_logic;
      z: out unsigned(0 to 1));
END incr;

ARCHITECTURE behav OF incr IS
BEGIN
  PROCESS(clk)
    VARIABLE count: unsigned(0 to 1);
  BEGIN
    IF rising_edge(clk) THEN
      IF en = '1' THEN
        count := count + 1;
      END IF;
    END IF;
    z <= count;
  END PROCESS;
END behav;
```




# Edge Sensitive D Flip-Flop

- ❑ Assignment on rising or falling edge of control signal (Clock)
  - **rising\_edge()** and **falling\_edge()** functions can be used to specify clock edge
- ❑ Memory inferred because “q” is not assigned for all cases

```
library IEEE;
use IEEE.std_logic_1164.all;

ENTITY d_ff is
  PORT(d      : IN  std_logic;
        clk   : IN  std_logic;
        q     : OUT std_logic;
        qn    : OUT std_logic);
END d_ff;

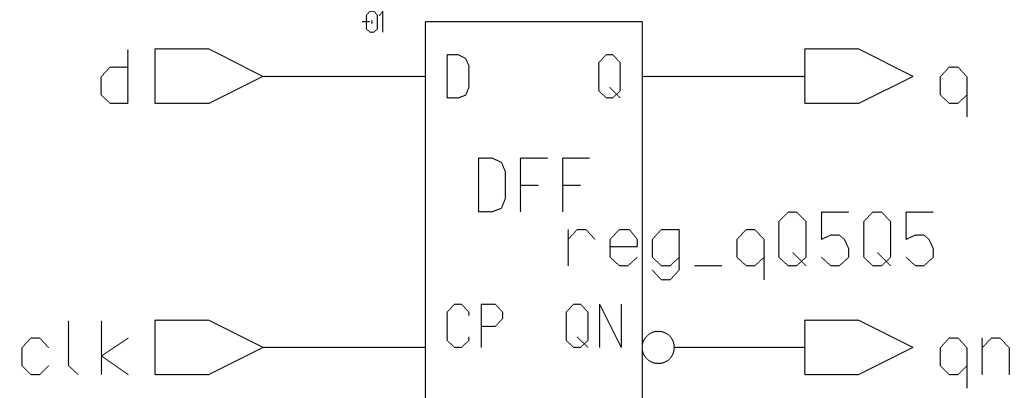ARCHITECTURE behavior OF d_ff IS
  BEGIN
    seq : PROCESS(clk)
      BEGIN
        IF(rising_edge(clk)) THEN
          q <= d;
        END IF;
      END PROCESS seq;
    qn <= not q;
  END behavior;
```




# Edge Sensitive D Flip-Flop with Synchronous Reset

- ❑ Synchronous reset, so only clk in sensitivity list
- ❑ Memory inferred because “q” is not assigned for all cases

```
library IEEE;
use IEEE.std_logic_1164.all;

ENTITY d_ff is
  PORT(d      : IN  std_logic;
        clk   : IN  std_logic;
        q     : OUT std_logic);
END d_ff;

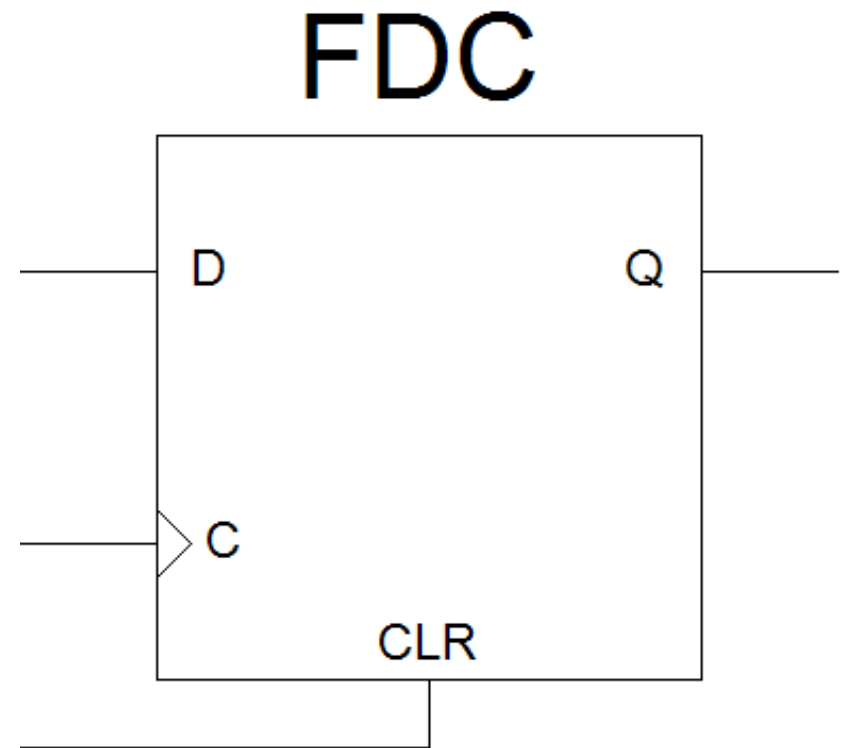ARCHITECTURE behav OF FlipFlop IS
BEGIN
  PROCESS(clk)
  BEGIN
    IF clk'event AND clk= '1' THEN
      IF reset = '0' THEN
        q <= '0';
      ELSE
        q <= d;
      END IF;
    END IF;
  END PROCESS;
END behav;
```




# Edge Sensitive D Flip-Flop with Asynchronous Reset

- ❑ The only signals in the process sensitivity list other than CLOCK should be asynchronous signals
- ❑ Memory inferred because “d” is not assigned for all cases

```
library IEEE;
use IEEE.std_logic_1164.all;

ENTITY d_ff is
    PORT(d      : IN  std_logic;
         clk    : IN  std_logic;
         q      : OUT std_logic);
END d_ff;

 ARCHITECTURE behav OF FlipFlop IS
BEGIN
    PROCESS(clk, reset)
    BEGIN
        IF reset = '0' THEN
            q <= '0';
        ELSIF clk'event AND clk= '1' THEN
            q <= d;
        END IF;
    END PROCESS;
END behav;
```



# A Few Coding Tips

## □ Modularity

- Write one module per file and name the file the same as the module.
- Break larger designs into modules on meaningful boundaries.
- Always use formal port mapping of sub-modules (named instantiation)
- Be careful to create correct sensitivity lists.

## □ Is your code for synthesis or simulation only?

- VHDL provides many ways of doing the same thing
- Some modules such as test benches, are never intended to be synthesized into actual hardware –in these types of modules, feel free to use the full monster that is VHDL

# Synthesis Considerations

- ❑ For modules you intend on synthesizing, you should apply a coding style to realize:
  - Efficiency
  - Predictability
  - Synthesizability
- ❑ Efficiency is important, for both performance and cost concerns
  - Use multiplication, division, and modulus operators sparingly
  - Use vectors / arrays to create “memories” only if you are sure the synthesis tool does it properly
  - CASE may be better than large IF-ELSE trees
  - Keep your mind focused on what hardware you are implying by your description



# Synthesis Considerations (cont.)

- ❑ Predictability is important
  - Predictability of what hardware may be created by what you describe
  - Predictability of hardware behavior
    - Hardware behavior will match your description.
    - No dependency on event ordering in code.
  - Use supplied templates!
- ❑ Realize that synthesis is automated mapping of your functionality based on various algorithms
  - Invariably limited capability
  - Garbage in, garbage (or errors) out
- ❑ Carefully read synthesis warnings and errors to identify problems you may be unaware of

# Questions?